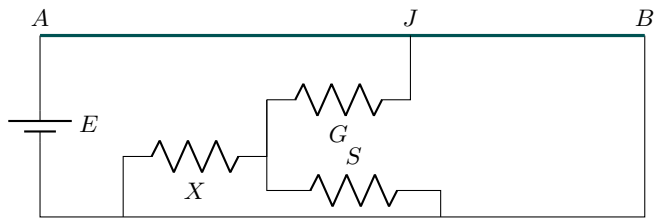


Low resistance by potentiometer



Compare balancing lengths for unknown resistance X and standard resistance S .